

- 10.4 Develop equations for the logical effort and parasitic delay with respect to the C_0 input of an n -stage Manchester carry chain computing $C_1 \dots C_n$. Consider all of the internal diffusion capacitances when deriving the parasitic delay. Use the transistor widths shown in Figure 10.87 and assume the P_i and G_i transistors of each stage share a single diffusion contact.

 


FIG 10.87 Manchester carry chain

- 10.5 Using the results of Exercise 10.4, what Manchester carry chain length gives the least delay for a long adder?
- 10.10 Write a Boolean expression for C_{out} in the circuit shown in Figure 10.6(b). Simplify the equation to prove that the pass-transistor circuits do indeed compute the majority function.

 


FIG 10.6 Transmission gate full adder

- 10.18 Table 10.12 and Figure 10.75 illustrated radix-4 Booth encoding using X_i , $2X_i$, and M_i . An alternative encoding is to use *POS*, *NEG*, and *DOUBLE*. *POS* is true for the multiples Y and $2Y$. *NEG* is true for the multiples $-Y$ and $-2Y$. *DOUBLE* is true for the multiples $2Y$ and $-2Y$. Design a Booth encoder and selector using this encoding.

Table 10.12 Radix-4 modified Booth encoding values						
Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	X_i	$2X_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	$-0 (= 0)$	0	0	1

 


FIG 10.75 Radix-4 Booth encoder and selector