 




VLSI Signal Processing

Lecture 9 Redundant Arithmetic






Redundant?

- A non-redundant radix- r number has digits from the set $\{0,1,\dots,r-1\}$ and all numbers can be represented in a **unique** way
- A radix- r redundant signed-digit number system is based on digit set $S \equiv \{-\beta, \dots, -1, 0, 1, \dots, \alpha\}$, where $1 \leq \beta, \alpha \leq r-1$
- The digit set S contains more than r values \rightarrow multiple representations for any number in signed digit format. Hence, the name **redundant**
- A **symmetric** signed digit has $\alpha = \beta$.
- **Carry-free addition** is one of the most attractive properties of redundant signed-digit numbers. This allows most significant digit (**MSD**) **first** redundant arithmetic, also called **on-line arithmetic** (division..)






1-1 onto Mapping?

 


r numbers

 

$\alpha+\beta+1$ elements

Digit set



 

Redundant Number Representations

- A **symmetric** signed-digit representation uses the digit set $D_{\langle r, \alpha \rangle} = \{-\alpha, \dots, -1, 0, 1, \dots, \alpha\}$, where r is the radix and α the largest digit in the set.

- A number in this representation is written as:

$$X_{\langle r, \alpha \rangle} = x_{W-1} \circ x_{W-2} \dots x_1 x_0 = \sum x_{W-1-i} r^i$$

- The **sign** of the number X is given by the sign of the most significant non-zero digit
- If $2\alpha + 1 < r$, the digit set $D_{\langle r, \alpha \rangle}$ is incomplete (i.e. some numbers cannot be represented)
- If $2\alpha + 1 = r$, the digit set $D_{\langle r, \alpha \rangle}$ is complete but not redundant
- If $2\alpha + 1 > r$, the digit set $D_{\langle r, \alpha \rangle}$ is redundant





Example


- Signed-Digit Numbers $X_{\langle r, \alpha \rangle} = x_{W-1} \circ x_{W-2} \dots x_1 x_0 = \sum x_{W-1-i} r^i$

$\{-1, 0, 1\}$

	1	1/2	1/4	
Represent	0	0	-1	← Canonic Signed Digit (CSD)
$-\frac{1}{4}$	0	-1	1	← 3 different
	-1	1	1	← Redundant

 Needs 2 bits since three numbers (-1,0,1)!





Review of Canonical Signed Digit

- Minimum number of non-zero bits
- A sequence of ones can be replaced with
 - A "-1" at the least significant position of the sequence
 - A "1" at the position to the left of the most significant position of the sequence
 - Zeros between the "1" and the "-1"
- Save more than 2/3 of the adder cells at an average





Redundant Characteristics

- Redundant factor
 - A measure of the redundancy of a symmetric signed-digit representations : $\rho = \alpha/(r-1)$

Digit Set $D_{\langle r, \alpha \rangle}$	α	Redundancy Factor ρ
Incomplete	$< (r - 1)/2$	$< \frac{1}{2}$
Complete but non-redundant	$= (r - 1)/2$	$= \frac{1}{2}$
Redundant	$\geq \lceil r/2 \rceil$	$> \frac{1}{2}$
Minimally redundant	$= \lceil r/2 \rceil$	$> \frac{1}{2}$ and < 1
Maximally redundant	$= r - 1$	$= 1$
Over-redundant	$> r - 1$	> 1





Redundancy Characteristic Example

Radix 4 with digit set $\{-2,-1,0,1,2\}$

$$\rho = \frac{\alpha}{r-1} = \frac{2}{3} \quad \rightarrow \quad \text{Minimally redundant}$$

Radix 4 with digit set $\{-3,-2,-1,0,1,2,3\}$

$$\rho = \frac{\alpha}{r-1} = \frac{3}{3} \quad \rightarrow \quad \text{Maximally redundant}$$





Carry-Free ?

- Redundant number representations **limit the carry propagation to a few bit-positions**, which is usually independent of the wordlength W .
- + and -

+

- Carry-free arithmetic
- independent of W
- MSD – first

1	1/2	1/4
0	0	-1
0	-1	1
-1	1	1

-

- Hard to find the sign
- More bits
- Conversion
- Not good for non-arithmetic





Radix-2 Signed-Digit Number

Each signed digit is represented by 2 bits

$\{-1, 0, 1\}$ 3 values \rightarrow 2 bits representation

X^+	X^-	X
0	0	0
0	1	-1
1	0	1
1	1	0

$$X = X^+ - X^-$$

Two unsigned binary numbers

Redundant





Redundant Arithmetic

- $X_{\langle r, \alpha \rangle} = X^+ - X^-$, $Y_{\langle r, \alpha \rangle} = Y^+ - Y^-$
- Hybrid radix-r addition $X_{\langle r, \alpha \rangle} + Y$
- Hybrid radix-r subtraction $X_{\langle r, \alpha \rangle} - Y$
- A signed-digit addition/subtraction can then be viewed as a **concatenation** of one hybrid addition/subtraction and one hybrid subtraction/addition





Hybrid Radix-2 Addition

Signed digit number $\{-1, 0, 1\}$

$$S_{\langle 2.1 \rangle} = X_{\langle 2.1 \rangle} + Y \leftarrow \text{unsigned}$$

where, $X_{\langle n,\alpha \rangle} = x_{W-1} \cdot x_{W-2} \cdot x_{W-3} \dots x_0$, $Y = y_{W-1} \cdot y_{W-2} \cdot y_{W-3} \dots y_0$. The addition is carried out in two steps:

1. The 1st step is carried out in parallel for all the bit positions. An intermediate sum $p_i = x_i + y_i$ is computed, which lies in the range $\{\bar{1}, 0, 1, 2\}$. The addition is expressed as:

$$x_i + y_i = 2t_i + u_i,$$

where t_i is the transfer digit and has value 0 or 1, and is denoted as t_i^+ ; u_i is the interim sum and has value either 1 or 0 and is denoted as $-u_i^-$. t_{-1} is assigned the value of 0.

2. The sum digits s_i are formed as follows:

$$s_i = t_{i-1}^+ - u_i^-$$





Hybrid Radix-2 Addition

Digit	Radix 2 Digit Set	Binary Code
x_i	$\{\bar{1}, 0, 1\}$	$x_i^+ - x_i^-$
y_i	$\{0, 1\}$	y_i^+ Plus-Plus-Minus
$p_i = x_i + y_i$	$\{\bar{1}, 0, 1, 2\}$	$2t_i + u_i$
u_i	$\{\bar{1}, 0\}$	$-u_i^-$
t_i	$\{0, 1\}$	t_i^+
$s_i = u_i + t_{i-1}$	$\{\bar{1}, 0, 1\}$	$s_i^+ - s_i^-$

Pass to the next level

$$s_i = t_{i-1}^+ - u_i^- \quad p_i = x_i + y_i = 2t_i + u_i$$


Binary code





Hybrid Radix-2 Adder

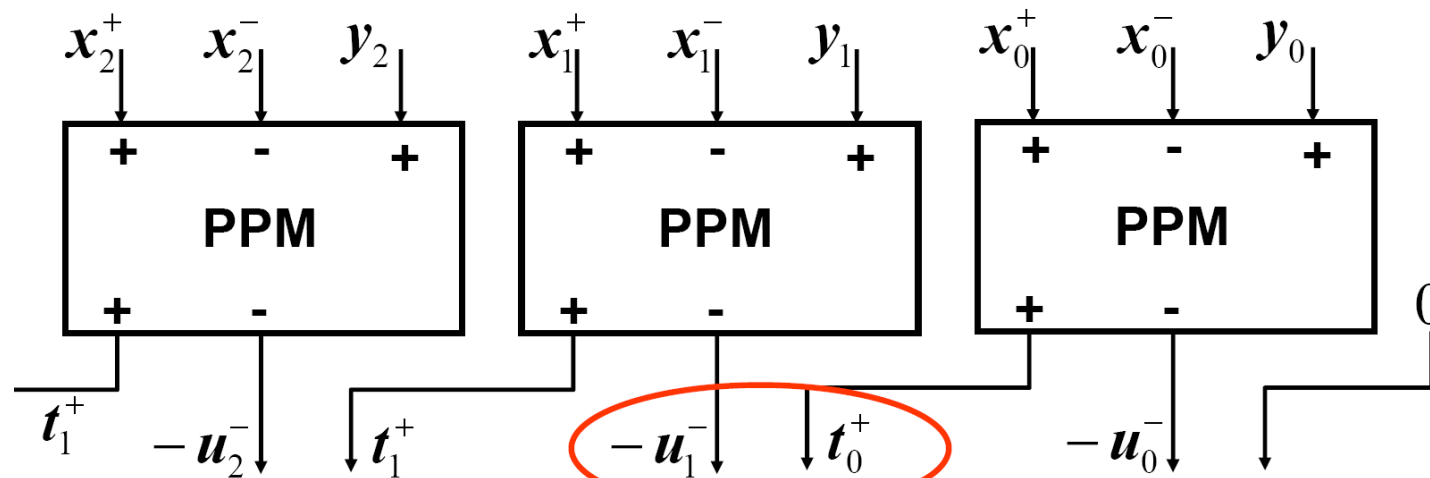- PPM: Plus-Plus-Minus adder (Full adder)



$$s_1 = s_1^+ - s_1^- = t_0^+ - u_1^-$$


No carry!





Example

- Eight-digit hybrid radix-2 adder

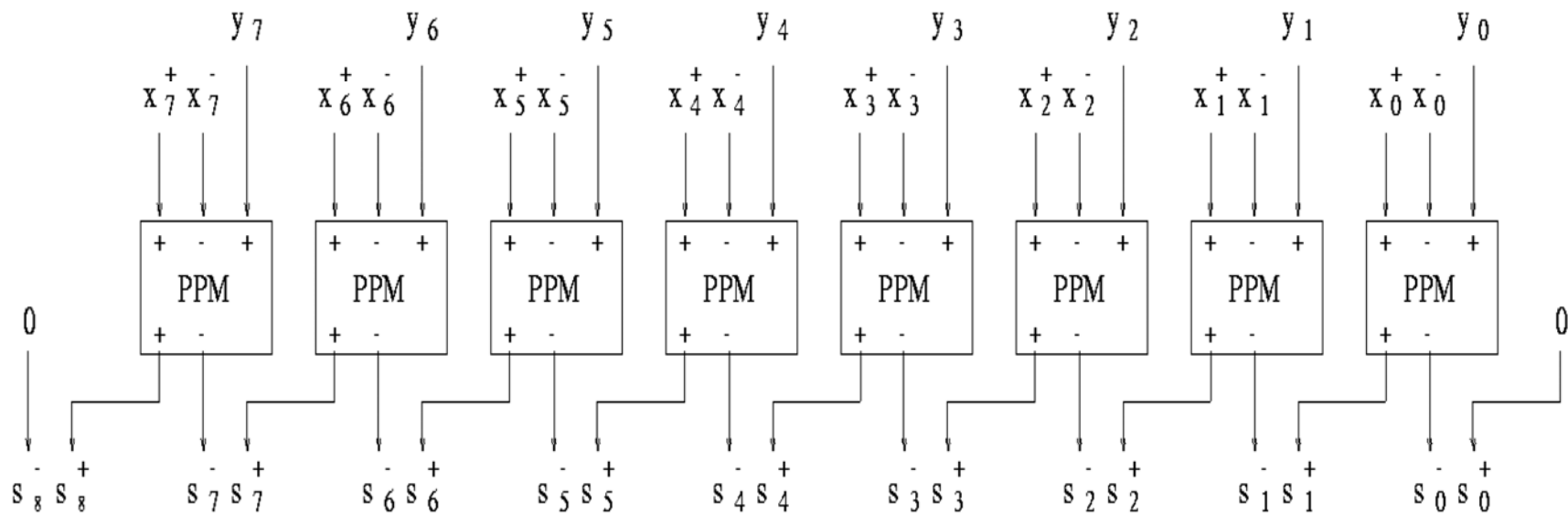

The sum has 9 digits !!







Digit-Serial Arithmetic, LSD

By Folding !!

Transfer digit delayed

 

Least Significant Digit
(LSD)
First

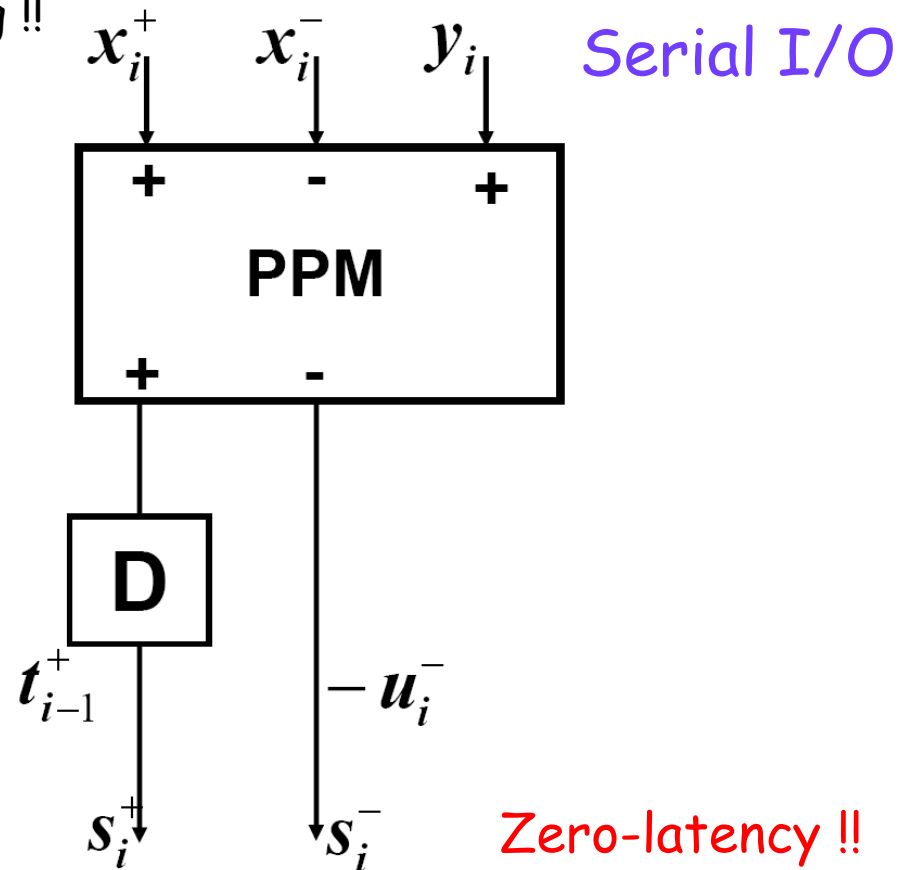

One 8-digit addition takes 9 clock cycles





Digit-Serial Arithmetic, MSD


interim sum digit
delayed

↓

Most Significant Digit
(MSD)
First

↓

Good for e.g. Division

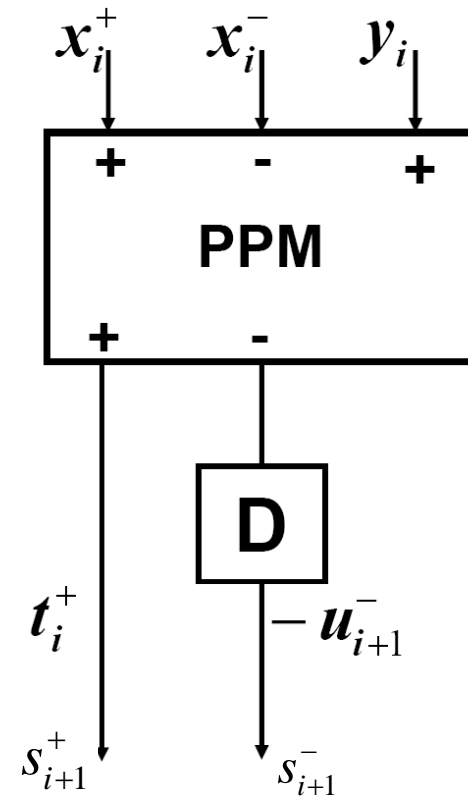

One clock cycle latency !!

Note: a zero digit needs to be inserted between 2 consecutive input operands





Hybrid Radix-2 Subtraction

Signed digit number $\{-1, 0, 1\}$

$$S_{\langle 2.1 \rangle} = X_{\langle 2.1 \rangle} - Y \leftarrow \text{unsigned}$$

where, $X_{\langle r.\alpha \rangle} = x_{W-1}x_{W-2}x_{W-3}\dots x_0$, $Y = y_{W-1}y_{W-2}y_{W-3}\dots y_0$. The subtraction is carried out in two steps :

1. The 1st step is carried out in parallel for all the bit positions. An intermediate difference $p_i = x_i - y_i$ is computed, which lies in the range $\{\bar{2}, \bar{1}, 0, 1\}$. The addition is expressed as:

$$x_i - y_i = 2t_i + u_i,$$

where t_i is the transfer digit and has value 1 or 0, and is denoted as $-t_i^-$; u_i is the interim sum and has value either 0 or 1 and is denoted as u_i^+ . t_{-1} is assigned the value of 0.

2. The sum digits s_i are formed as follows:

$$s_i = -t_{i-1}^- + u_i^+$$





Hybrid Radix-2 Subtraction

Digit	Radix 2 Digit Set	Binary Code
x_i	$\{\bar{1}, 0, 1\}$	$x_i^+ - x_i^-$
y_i	$\{0, 1\}$	y_i^-
$p_i = x_i - y_i$	$\{\bar{2}, \bar{1}, 0, 1\}$	$2t_i + u_i$
u_i	$\{0, 1\}$	u_i^+
t_i	$\{\bar{1}, 0\}$	$-t_i^-$
$s_i = u_i + t_{i-1}$	$\{\bar{1}, 0, 1\}$	$s_i^+ - s_i^-$

Minus-Minus-Plus

Pass to the next level

$$s_i = -t_{i-1}^- + u_i^+$$

Use negative transfer digit !!



Remarks



- $\{-1, 0, 1\} - \{0, 1\} = \{-2, -1, 0, 1\}$

$$x_i = x_i^+ - x_i^- \quad y_i$$

$$\begin{cases} 1 = u_i^+ \\ 0 \\ -1 = -2t_i^- + u_i^+ \\ -2 = -2t_i^- \end{cases}$$


Pass to the next level





Hybrid Radix-2 Subtractor

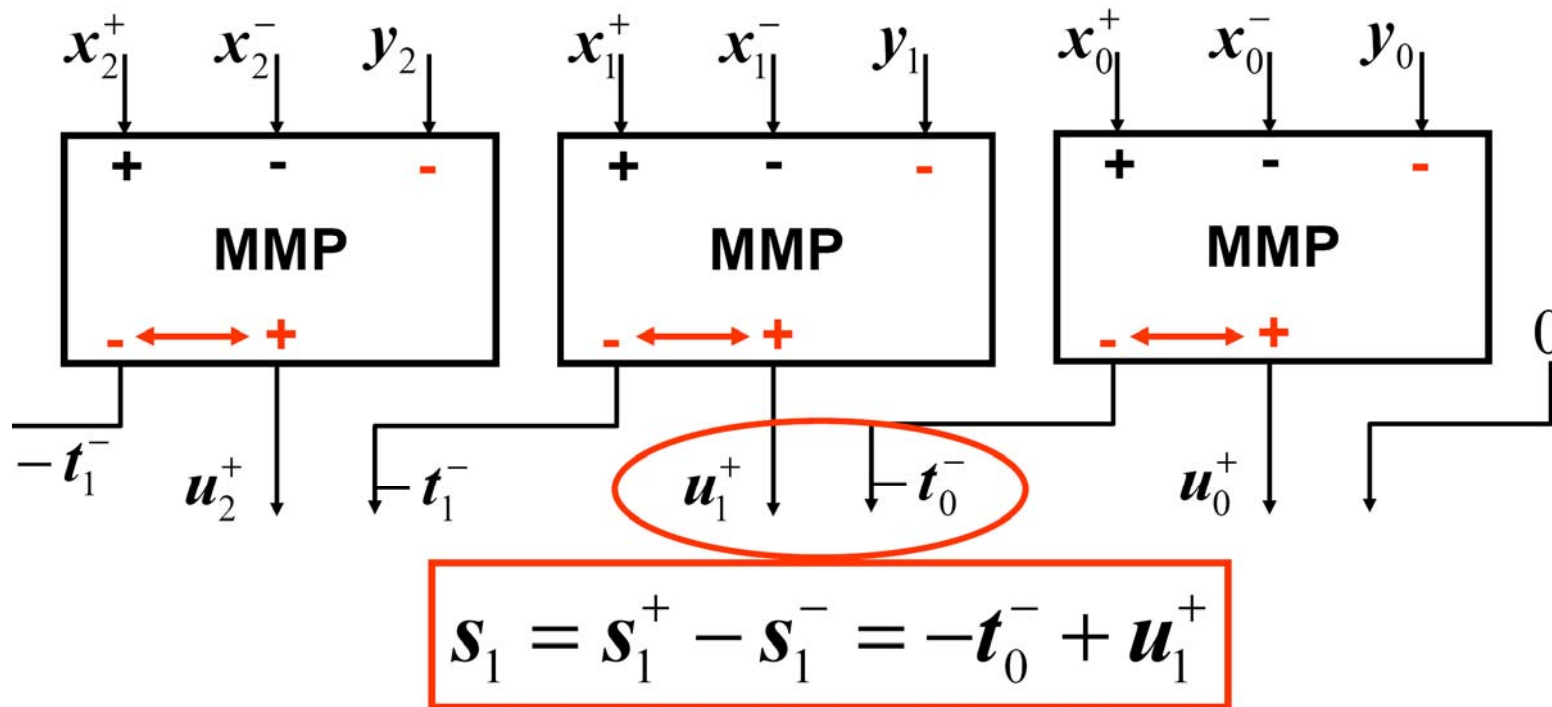
- MMP: Minus-Minus-Plus adder (Full adder)






Example

- Eight-digit hybrid radix-2 subtractor

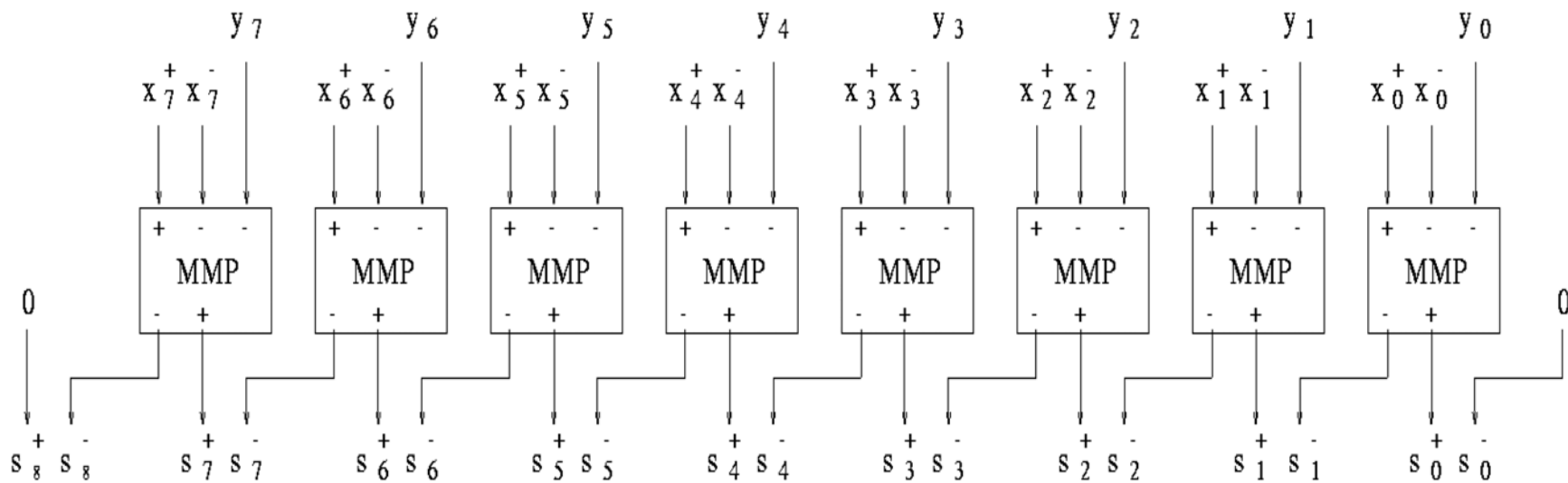

Hybrid Radix-2 Addition/Subtraction

 

$A/S_{bar} = 1$ for addition, $A/S_{bar} = 0$ for subtraction



Signed-Binary Digit (SBD) Arithmetic



- $Y_{\langle r, \alpha \rangle} = Y^+ - Y^-$, is a signed digit number, where Y^+ and Y^- are from the digit set $\{0, 1, \dots, \alpha\}$.
- A signed digit number is thus subtraction of 2 unsigned conventional numbers.
- Signed addition is given by:

$$\begin{aligned} S_{\langle r, \alpha \rangle} &= X_{\langle r, \alpha \rangle} + Y_{\langle r, \alpha \rangle} = X_{\langle r, \alpha \rangle} + Y^+ - Y^-, \\ \Rightarrow S1_{\langle r, \alpha \rangle} &= X_{\langle r, \alpha \rangle} + Y^+, \\ S_{\langle r, \alpha \rangle} &= S1_{\langle r, \alpha \rangle} - Y^- \end{aligned}$$

- Digit serial SBD adders can be derived by folding the digit parallel adders in both lsd-first and msd-first modes.
- LSD-first adders have zero latency and msd-first adders have latency of 2 clock cycles.






Signed Binary Digit Arithmetic

- $Y_{\langle r, \alpha \rangle} = Y^+ - Y^-$, is a signed digit number, where Y^+ and Y^- are (unsigned conventional numbers) from the digit set $\{0, 1, \dots, \alpha\}$.
- Signed addition is given by


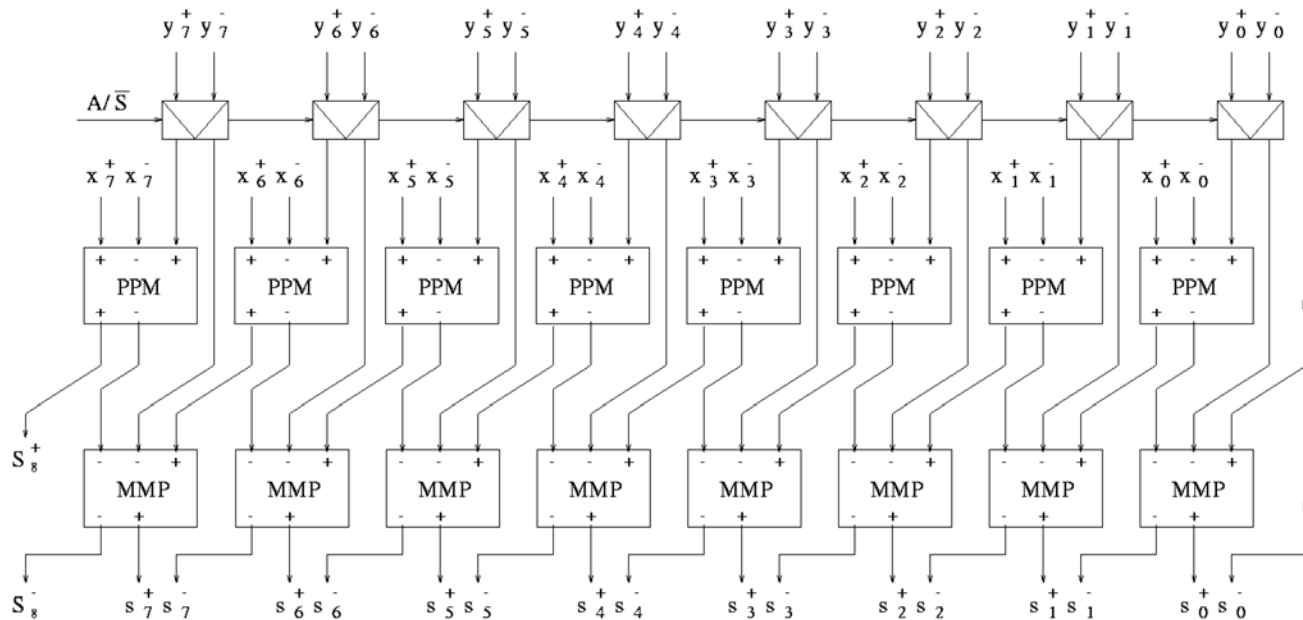
$$S_{\langle r, \alpha \rangle} = X_{\langle r, \alpha \rangle} + Y_{\langle r, \alpha \rangle} = (X_{\langle r, \alpha \rangle} + Y^+) - Y^-$$





Remarks

  - Signed-digit addition can be viewed as a concatenation of one hybrid addition and one hybrid subtraction.
- Digit-serial redundant adders can be derived by folding methodology (LSD-first, or MSD-first)
- LSD-first adders have zero latency, while MSD-first adders have 2 clock cycles latency.





Hybrid Radix-4 Addition

- Higher order radices can be employed to reduce the number of iteration cycles.
- Maximally redundant hybrid radix-4 addition (MRHY4A) considers the numbers based on digit set $D_{\langle 4,3 \rangle} = \{-3, -2, -1, 0, 1, 2, 3\}$, $\rho = 1$
- Minimally redundant hybrid radix-4 addition (mrHY4A) considers the numbers based on digit set $D_{\langle 4,2 \rangle} = \{-2, -1, 0, 1, 2\}$, $\rho = 2/3$





MRHY4A

$$S_{\langle 4.3 \rangle} = X_{\langle 4.3 \rangle} - Y_4 \leftarrow \text{unsigned}$$

- The first step computes:

$$x_i + y_i = 4t_i + u_i$$

Replacing the respective binary codes from the table the following is obtained :

$$(2x_i^{+2} - 2x_i^{-2} + 2y_i^{+2}) + x_i^+ - x_i^- + y_i^+ = 4t_i^+ + 2u_i^{+2} - 2u_i^{-2} - u_i^-$$

A MRHY4A cell consisting of two PPM adders is used to compute the above.

- Step 2 computes computes $s_i = t_{i-1} + u_i$. Replacing s_i , u_i , and t_{i-1} by corresponding binary codes leads to $s_i^{+2} = u_i^{+2}$, $s_i^{-2} = u_i^{-2}$, $s_i^+ = t_{i-1}^+$ and $s_i^- = u_i^-$.





Digit Sets in MRHR4A

$$D_{\langle 4,3 \rangle} = \{-3, -2, -1, 0, 1, 2, 3\},$$

Digit	Radix 4 Digit Set	Binary Code
x_i	$\{\bar{3}, \bar{2}, \bar{1}, 0, 1, 2, 3\}$	$2x_i^{+2} - 2x_i^{-2} + x_i^+ - x_i^-$
y_i	$\{0, 1, 2, 3\}$	$2y_i^{+2} + y_i^+$
$p_i = x_i + y_i$	$\{\bar{3}, \bar{2}, \bar{1}, 0, 1, 2, 3, 4, 5, 6\}$	$4t_i + u_i$
u_i	$\{\bar{3}, \bar{2}, \bar{1}, 0, 1, 2\}$	$2u_i^{+2} - 2u_i^{-2} - u_i^-$
t_i	$\{0, 1\}$ <i>Pass to the next level</i>	t_i^+
$s_i = u_i + t_{i-1}$	$\{\bar{3}, \bar{2}, \bar{1}, 0, 1, 2, 3\}$	$2s_i^{+2} - 2s_i^{-2} + s_i^+ - s_i^-$

PPM

$$x_i + y_i = p_i = 4t_i + u_i$$


$$s_i = u_i + t_{i-1}, \text{ where } s_i^{+2} = u_i^{+2}, s_i^{-2} = u_i^{-2}, s_i^+ = t_{i-1}^+, s_i^- = u_i^-$$





MRHY4A Adder Cell

Step 1

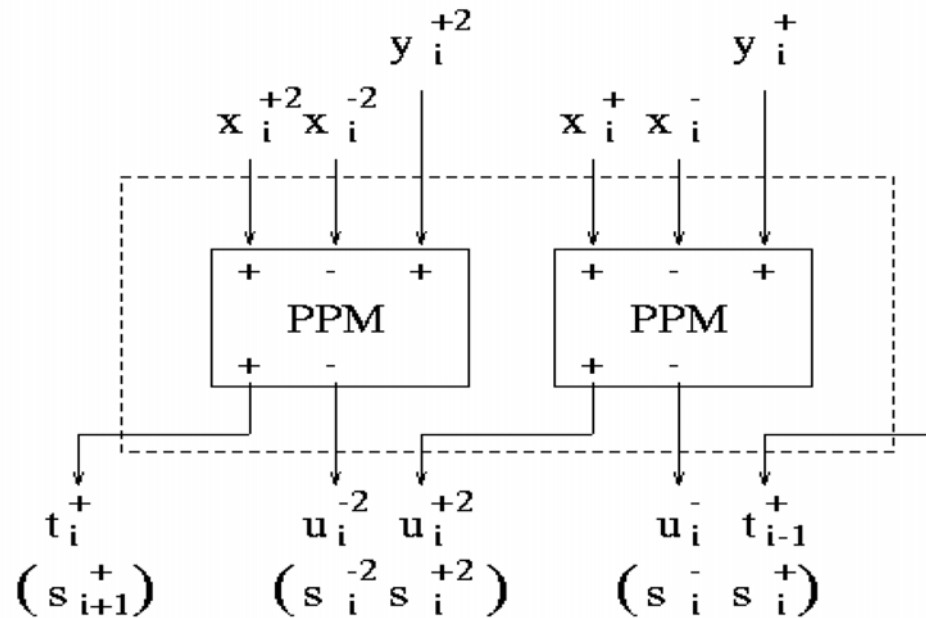


2PPM (full) adders that perform the 2 grouped additions in parallel and reduce the number of bits from 6 to 4 with the weights.





4-Digit MRHY4A

 



mrHY4A

$$S_{\langle 4.2 \rangle} = X_{\langle 4.2 \rangle} + Y_4 \leftarrow \text{unsigned}$$

- The first step computes:

$$x_i + y_i = 4t_i + u_i$$

Replacing the respective binary codes from the table the following is obtained :

$$(-2x_i^{-2} + 2y_i^{+2}) + (x_i^+ + x_i^{++} + y_i^+) = 4t_i^+ - 2u_i^{-2} + u_i^+$$

A mrHY4A cell consisting of one PPM adder and a full adder is used to compute the above.

- Step 2 computes computes $s_i = t_{i-1} + u_i$. Replacing s_i , u_i , and t_{i-1} by corresponding binary codes leads to $s_i^{-2} = u_i^{-2}$, $s_i^{++} = t_{i-1}^+$ and $s_i^+ = u_i^+$.





Digit Sets in mrHY4A

$$D_{\langle 4,2 \rangle} = \{-2, -1, 0, 1, 2\}$$

The digit number is represented by 3 bits !!

Digit	Radix 4 Digit Set	Binary Code
x_i	$\{\bar{2}, \bar{1}, 0, 1, 2\}$	$-2x_i^{-2} + x_i^+ + x_i^{++}$
y_i	$\{0, 1, 2, 3\}$	$2y_i^{+2} + y_i^+$
$p_i = x_i + y_i$	$\{\bar{2}, \bar{1}, 0, 1, 2, 3, 4, 5\}$	$4t_i + u_i$
u_i	$\{\bar{2}, \bar{1}, 0, 1\}$	$-2u_i^{-2} + u_i^+$
t_i	$\{0, 1\}$	t_i^+
$s_i = u_i + t_{i-1}$	$\{\bar{2}, \bar{1}, 0, 1, 2\}$	$2s_i^{-2} + s_i^+ + s_i^{++}$

Full adder

Pass to the next level



$$x_i + y_i = p_i = 4t_i + u_i$$

$$s_i = u_i + t_{i-1}$$



Minimally redundant Hybrid Radix-4 Adder Cell


Carry within cell

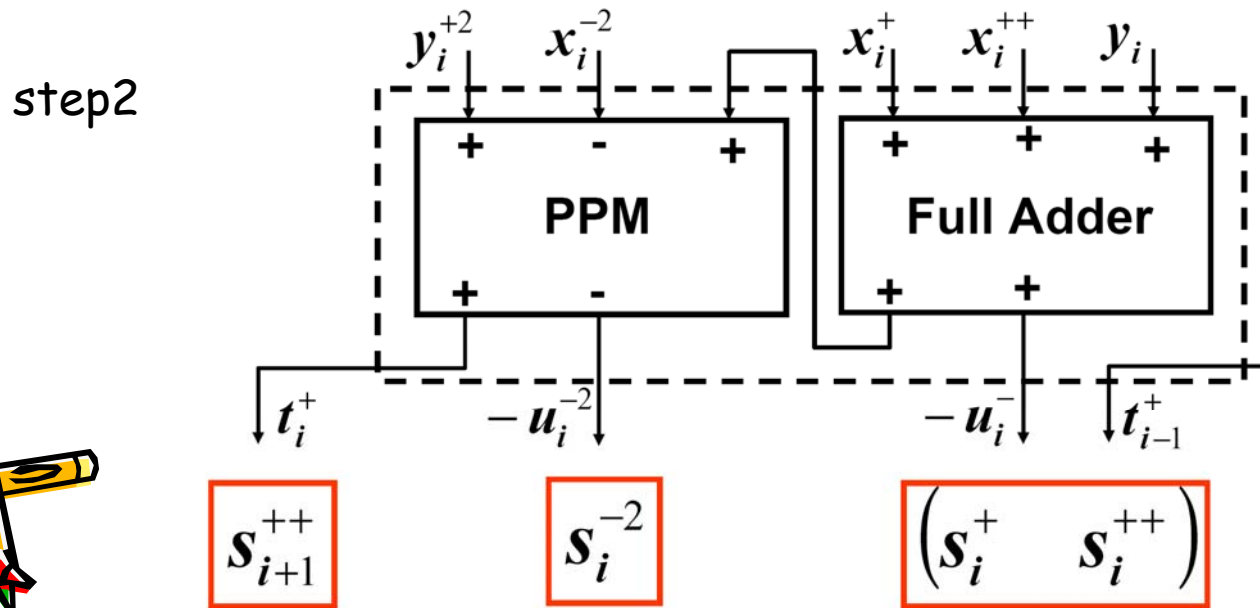 

Non-Redundant to Redundant Conversion



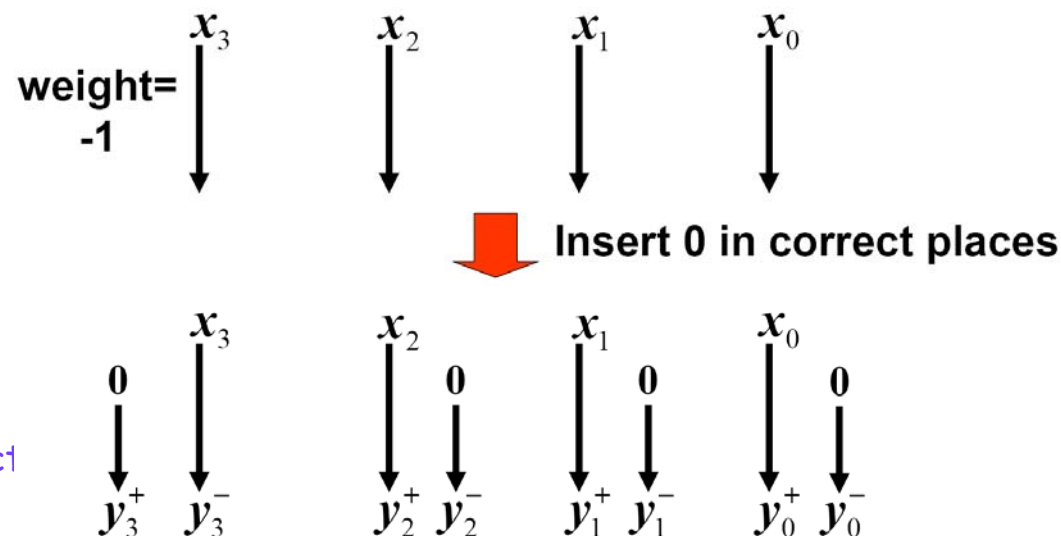
- The non-redundant input digit set can be considered as a subset of the redundant input digit set.
- Radix-2 representation:
 - A non-redundant number $X = x_3 \circ x_2 x_1 x_0$ can be converted to a redundant number $Y = y_3 \circ y_2 y_1 y_0$, where each digit y_i is encoded as y_i^+ and y_i^- as shown below



Non-Redundant to Redundant Conversion



 
- Radix-4 representation
 - X is a radix-4 complement number, whose digits x_i 's are encoded using 2 wires as $x_i = 2x_i^{+2} + x_i^+$. Its corresponding **maximally redundant number** Y is encoded using $y_i = 2y_i^{+2} - 2y_i^{-2} + y_i^+ - y_i^-$. The sign digit x_3 can take values $-3, -2, -1, \text{ or } 0$, and is encoded using $x_3 = -2x_3^{-2} - x_3^-$.





- radix-4 minimally redundant number: X is a radix-4 complement number, whose digits x_i are encoded using 2 wires as $x_i = 2x_i^{+2} + x_i^+$. Its corresponding minimally redundant number Y is encoded using $y_i = -2y_i^{-2} + y_i^+ + y_i^{++}$. To convert radix- r number x to redundant number $y_{\langle r, \alpha \rangle}$, the digits in the range $[\alpha, r - 1]$ are encoded using a transfer digit 1 and a corresponding digit $x_i - r$ where x_i is the i^{th} digit of x . Thus,
 
$$\begin{aligned} 2x_i^{+2} + x_i^+ &= 4x_i^{+2} - 2x_i^{+2} + x_i^+ \\ &= y_{i+1}^{++} - 2y_i^{-2} + y_i^+ \end{aligned}$$



Redundant to NonRedundant Converter



- In general, it is not possible to know the value of any of nonredundant digits until the least significant redundant digit become available

- Example

$$- 1000\overline{1} \longrightarrow (03333)_4$$

$$- 10001 \longrightarrow (10001)_4$$


To change the least significant digit from -1 to 1 causes all of the preceding (more significant) digits to be changed





Redundant to Non-red Conversion

 In general not possible to output ANY digit until LSD has been processed, i.e. advantage of MSD first "removed"



Introduces Carry-ripple

If a redundant number is scanned msd-first and transformed to a nonredundant radix-4 format

